

Experiment 7

The R-C Circuit

by
Austin Haggard

Experiment Performed: 3/18/15
Report Submitted: 3/25/15

Lab Partner:
Daniela Freire

GSA:
C. Monroe

Introduction:

In this lab we created a series circuit with a resistor and capacitor. We then unhooked the power source and measured the voltage drop over time using logger pro. A time constant was also calculated. Part two was skipped in this experiment due to missing equipment in the lab. Part three of this experiment we used the oscilloscope to measure a different time constant.

Data Analysis:

Part 1

Our theoretical time is going to be 10 seconds because that was the time measured. We then have to calculate the experimental value of time using the C value given to us by logger pro in our graph. To do this we use the equation below:

$$\frac{1}{C} = T_e$$
$$\frac{1}{.1499} = 6.67$$

Part 3

During Part three we first need to calculate the theoretical value of our time constant. This would be found by using the equation below:

$$C * F$$
$$1 * 10^{-10} * 10000 = 10^{-6}$$

Then to calculate the experimental value we measure to about 60% of the height of the wave and multiply this by the capacitance. Sample equation below:

$$R * C = T_e$$
$$50 * 10^{-6} = 5 * 10^{-5}$$

Then we had to propagate error to later assist in finding sigma d. This is done by using the equation below.

$$\sqrt{\sum E^2}$$
$$\sqrt{.1^2 + .01^2} = .1$$

To find the difference all we do is subtract the theoretical and experimental values.

$$T - E = d$$
$$10^{-7} - 5 * 10^{-5} = 4.9 * 10^{-5}$$

Then to find sigma D we take the square root of errors to the power of two.

$$\sqrt{\sum E^2}$$
$$\sqrt{.1^2 + .01^2} = .1$$

To find percent difference we use the following equation:

$$\frac{d}{E} * 100$$
$$\frac{.000049}{.00005} * 100 = 2\%$$

Figure 1: Shark Wave

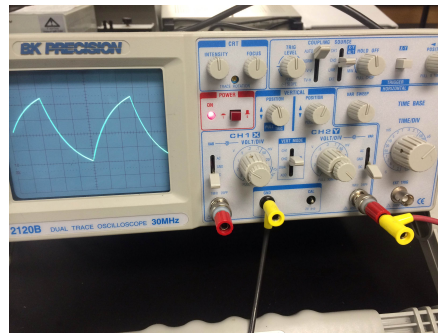


Figure 2: Switched Display

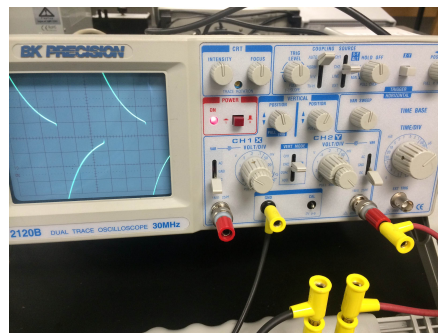


Table of Results:

Experimental: .00005	Theoretical: .000001
Discrepancy: .000049	Percent Difference: 2%

Discussion:

In this experiment we measured voltage across capacitors and resistors in different ways. In both of these experiments we found a time constant that we compared to a theoretical value. The largest error in this experiment would be resistances that are unaccounted for such as the wires and built in errors for the resistors. This would be an intrinsic random error because it the error can either be positive or negative and can't be fixed. In part 3 of this experiment it was found that when resistance is added to the circuit the slope of the oscilloscope graph decreases. Adding capacitance also decreases the slope. The relationship between V_c and V_r is that $V_c + V_r = V_0$. The third experiment was a success because d is less than σ_d .

Conclusion:

In this lab we looked at the effect of capacitance in a circuit. We adjusted the capacitance a resistance and also plotted graphs of the decay of power. This experiment was a success because our d was less than our σd .